

```

/*module for the aoi-gate of figure 4.3 instantiating
the gate primitives - fig4.4*/
module aoi_gate(o,a1,a2,b1,b2);
input a1,a2,b1,b2;// a1,a2,b1,b2 form the input
//ports of the module
output o;//o is the single output port of the module
wire o1,o2;//o1 and o2 are intermediate signals
//within the module
and g1(o1,a1,a2); //The AND gate primitive has two
and g2(o2,b1,b2);// instantiations with assigned
//names g1 & g2.
nor g3(o,o1,o2);//The nor gate has one instantiation
//with assigned name g3.
endmodule

```

```

//Test-bench for the aoi_gate above
module aoi_st;
reg a1,a2,b1,b2;
//specific values will be assigned to a1,a2,b1,
// and b2 and these connected
//to input ports of the gate insatntiations;
//hence these variables are declared as reg
wire o;
initial
begin

```

```

    a1 = 0;
    a2 = 0;
    b1 = 0;
    b2 = 0;
#3 a1 = 1;
#3 a2 = 1;
#3 b1 = 1;
#3 b2 = 0;
#3 a1 = 1;
#3 a2 = 0;
#3 b1 = 0;

```

```

end
initial #100 $stop;//the simulation ends after
//running for 100 tu's.
initial $monitor($time , " o = %b , a1 = %b ,
a2 = %b , b1 = %b , b2 = %b ",o,a1,a2,b1,b2);
aoi_gate gg(o,a1,a2,b1,b2);
endmodule

```

Figure 4.4 Module for the AOI gate of Figure 4.3 and a test bench for the same.